

Course 2032

Semester II

Theory

4 Credits

# Electric Circuits and Systems

A complete syllabus-aligned handbook with clear explanations, practical or exam guidance, Malayalam-support notes, diagrams, activities and revision tools.

|                 |                                                                                                                                       |  |                |
|-----------------|---------------------------------------------------------------------------------------------------------------------------------------|--|----------------|
| Programmes      | <b>Electrical &amp; Electronics Engineering, Electrical Engineering and Electrical Engineering &amp; Electric Vehicles Technology</b> |  |                |
| Contact hours   |                                                                                                                                       |  | <b>60</b>      |
| Teaching scheme |                                                                                                                                       |  | <b>4:0:0:0</b> |
| Credits         |                                                                                                                                       |  | <b>4</b>       |
| CIE / ESE       | <b>Theory CIE 40 / Theory ESE 60</b>                                                                                                  |  |                |
| Self-learning   | <b>6 h/week; 90 h total</b>                                                                                                           |  |                |

## Official Source Declaration and Verified Inconsistencies

This handbook is based only on the supplied official **Diploma Curriculum Revision 2026** syllabus PDF for Course **2032**, titled **Electric Circuits and Systems**. Objectives, course outcomes, teaching scheme, major topics, detailed coverage, activities and assessment are drawn from that source.

**Source treatment:** PDF table wrapping can interrupt a heading across lines. In such cases, this handbook retains the official intent in a clearly labelled topic. Normal teaching explanations, study flows, diagrams and Malayalam-support boxes are handbook support rather than claims of official wording.

**Verified source note:** No web research was used to establish syllabus content. Official references and URLs appear only where they are listed in the supplied PDF.

## COURSE DASHBOARD

## What You Are Expected to Learn

**60**

Contact hours

**4**

Credits

**Theory CIE 40**

CIE

**Theory ESE 60**

ESE

### Course introduction

Electric Circuits and Systems develops calculation and representation skills for DC network laws/theorems, AC series and parallel circuits, resonance and balanced three-phase systems. It requires clear phasor, waveform and circuit reasoning.

**Malayalam support:** □ handbook □□□□□□□□□□ syllabus topic □□□□ □□□□□□□□; □□□□□□□□ principle, diagram/procedure, application, common mistake □□□□□ □□□□□□□□ □□□□□□□□.

## Prerequisite foundation

Fundamentals of Engineering Mathematics (1002) and Basic Electrical & Electronics Engineering (1031).

Use prerequisites only as a revision bridge. The current course outcomes and detailed syllabus define the required performance.

## Teaching and assessment scheme

| L | T | P | S | Self-learning/week   | Contact hours | Credits | CIE           | ESE           |
|---|---|---|---|----------------------|---------------|---------|---------------|---------------|
| 4 | 0 | 0 | 0 | 6 h/week; 90 h total | 60            | 4       | Theory CIE 40 | Theory ESE 60 |

## STUDY METHOD

## How to Use This Handbook

## 1 · Understand

Read terms, conditions and purpose; make a short definition in your own words.

## 2 · Visualise

Follow the diagram, circuit, flow or procedure and label it accurately.

### 3 • Apply

Use the method block, calculation or practical checklist without skipping units or safety checks.

## 4 • Revise

Use questions, quick cards and common-mistake notes before examination.

### OFFICIAL STATEMENTS

## Objectives and Course Outcomes

### Official course objectives

1. Use basic laws and theorems to solve circuits.
2. Analyse AC series and parallel circuits.
3. Calculate resonance and parallel-AC parameters.
4. Analyse three-phase systems and interconnections.

### Student-friendly meaning

You should be able to recognise the relevant system or material, explain its principle, communicate through a correct diagram/table where needed and follow a defensible solution or practical method.

**Malayalam support:** CO പരീക്ഷാ exam-ൽ പരീക്ഷാ പരീക്ഷാ പരീക്ഷാ പരീക്ഷാ പരീക്ഷാ. Define, explain, apply പരീക്ഷാ action words പരീക്ഷാപരീക്ഷാ.

### Official Course Outcomes

| CO  | Official outcome                                                                  | Bloom level |
|-----|-----------------------------------------------------------------------------------|-------------|
| CO1 | Solve electric circuits using basic laws and network theorems.                    | Apply       |
| CO2 | Apply AC-series-circuit knowledge for different loads.                            | Apply       |
| CO3 | Apply resonance and methods for AC parallel circuits.                             | Apply       |
| CO4 | Calculate three-phase balanced-system parameters with different interconnections. | Apply       |

## Official CO-PO articulation matrix

| CO  | PO1 | PO2 | PO3 | PO4 | PO5 | PO6 | PO7-PO11 |
|-----|-----|-----|-----|-----|-----|-----|----------|
| CO1 | 3   | 2   | 2   | 2   | 2   | -   | -        |
| CO2 | 3   | 2   | 2   | 2   | 2   | -   | -        |
| CO3 | 3   | 2   | 2   | 2   | 2   | -   | -        |
| CO4 | 3   | 2   | 2   | 2   | 2   | -   | -        |

## SYLLABUS COVERAGE

### Curriculum Coverage Map

#### All official major topics mapped to handbook chapters

| Module | Title                                  | Official major topics                                                                                                                            | Hours                | CO  | Handbook section |
|--------|----------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------|----------------------|-----|------------------|
| 1      | Electric Circuits and Network Theorems | Circuit types/terms, Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta conversion.                                            | 3.5 L + 11.5 T hours | CO1 | Module 1         |
| 2      | Phasor Algebra and AC Series Circuits  | j operator, phasor rectangular/polar conversion and operations; pure R/L/C, RL/RC/RLC, impedance, power and power factor.                        | 10 L + 5 T hours     | CO2 | Module 2         |
| 3      | Resonance and Parallel AC Circuits     | Series resonance, Q factor and bandwidth; admittance/conductance/susceptance; two-branch parallel circuits; parallel resonance and applications. | 7 L + 8 T hours      | CO3 | Module 3         |
| 4      | Three-Phase AC Systems                 | Three-phase generation/waveforms/phasors/sequence; star/delta connections; balanced-system calculations and power.                               | 9.5 L + 5.5 T hours  | CO4 | Module 4         |

## LEARNING ROADMAP

### How the Modules Connect

#### Electric Circuits and Network Theorems

Circuit types/terms, Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta conversion.

CO1 · 3.5 L + 11.5 T hours

## Phasor Algebra and AC Series Circuits

j operator, phasor rectangular/polar conversion and operations; pure R/L/C, RL/RC/RLC, impedance, power and power factor.

CO2 · 10 L + 5 T hours

## Resonance and Parallel AC Circuits

Series resonance, Q factor and bandwidth; admittance/conductance/susceptance; two-branch parallel circuits; parallel resonance and applications.

CO3 · 7 L + 8 T hours

## Three-Phase AC Systems

Three-phase generation/waveforms/phasors/sequence; star/delta connections; balanced-system calculations and power.

CO4 · 9.5 L + 5.5 T hours

### MODULE 1

## Electric Circuits and Network Theorems

Circuit types/terms, Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta conversion.

3.5 L + 11.5 T hours

CO1

Understand · Apply

### Learning goals


Identify core terms, explain the principle and complete the stated application or practical outcome.

### Key evidence

Use a labelled diagram, table, graph, procedure or calculation that matches the topic.
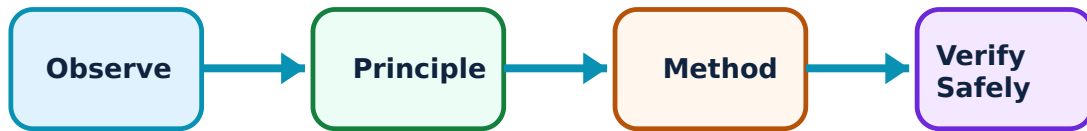
## Engineering habit

Check units, polarity/direction, ratings, materials and safety before concluding.



Study flow for Electric Circuits and Network Theorems: identify the system, state its principle, follow the correct method and verify the result safely.

### 1. Circuit fundamentals and Kirchhoff laws–

Circuit analysis uses branch, node, loop, current, voltage, source and reference direction consistently. Kirchhoff's current law expresses charge conservation at a node; Kirchhoff's voltage law expresses algebraic voltage balance around a loop.

#### Study and application method

Assign current/voltage directions, write equations with a consistent sign convention, solve maximum-three-loop systems and interpret negative result as reversed assumed direction.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

#### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Assign current/voltage directions, write equations with a consistent sign convention, solve maximum-three-loop systems and interpret negative result as reversed assumed direction.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതെങ്കിലും concept എഴുതുക. ഏതെങ്കിലും diagram / circuit / formula / procedure എഴുതുക. ഏതെങ്കിലും result എഴുതുക. application എഴുതുക. Technical terms English-  
എഴുതുക.

**Common mistake / precaution:** Do not mix reference directions midway through an equation set.

## 2. Mesh and nodal analysis–

Mesh analysis uses loop currents; nodal analysis uses node voltages. Both transform a circuit into simultaneous equations and are limited to the stated complexity in the syllabus.

### Study and application method

Choose method that gives fewer unknowns, label circuit clearly, write independent equations and verify one result using KCL/KVL.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.



## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Choose method that gives fewer unknowns, label circuit clearly, write independent equations and verify one result using KCL/KVL.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഉപയോഗിക്കണം. ഏതു diagram / circuit / formula / procedure ഉപയോഗിക്കണം. ഏതു result ഉപയോഗിക്കണം application ഉപയോഗിക്കണം. Technical terms English-ൽ എഴുതണം.

**Common mistake / precaution:** A current source or voltage source may require special treatment; identify it before writing equations.

## 3. Network theorems and star-delta conversion–

Superposition, Thevenin, Norton and maximum-power-transfer theorems simplify linear-network analysis. Star-delta conversion replaces a three-terminal network with an equivalent form for simple DC circuits.

### Study and application method

State theorem, deactivate only independent sources where appropriate, determine equivalent seen at load terminals and then restore load/result.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** State theorem, deactivate only independent sources where appropriate, determine equivalent seen at load terminals and then restore load/result.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ problem ഈ സാഹചര്യത്തിൽ. ഈ diagram / circuit / formula / procedure ഈ problem ഈ സാഹചര്യത്തിൽ. ഈ result ഈ application ഈ സാഹചര്യത്തിൽ ഈ സാഹചര്യത്തിൽ. Technical terms English-  
ഈ ഈ.

**Common mistake / precaution:** Superposition applies to voltage/current, not directly to power; calculate power after final response.

**Module 1 revision cue:** Re-read official major topics, redraw one key diagram/flow and explain one practical or numerical method without looking at notes.

## MODULE 2

# Phasor Algebra and AC Series Circuits

$j$  operator, phasor rectangular/polar conversion and operations; pure R/L/C, RL/RC/RLC, impedance, power and power factor.

10 L + 5 T hours

CO2

Understand · Apply

## Learning goals

Identify core terms, explain the principle and complete the stated application or practical outcome.

## Key evidence

Use a labelled diagram, table, graph, procedure or calculation that matches the topic.

## Engineering habit

Check units, polarity/direction, ratings, materials and safety before concluding.



Study flow for Phasor Algebra and AC Series Circuits: identify the system, state its principle, follow the correct method and verify the result safely.

## 1. Phasors and complex-number representation–

A phasor represents sinusoidal magnitude and phase at common frequency. The  $j$  operator represents a ninety-degree rotation. Rectangular and polar forms support different calculations.

### Study and application method

Convert consistently between forms, add/subtract in rectangular form and multiply/divide in polar form, then state final magnitude/angle.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Convert consistently between forms, add/subtract in rectangular form and multiply/divide in polar form, then state final magnitude/angle.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ ചോദ്യത്തിന് ഉപയോഗിക്കണം. ഈ diagram / circuit / formula / procedure ഉപയോഗിക്കണം. ഏതു result ഉണ്ടാകും എന്നതിനെക്കുറിച്ച് application ഉപയോഗിച്ച് വിശദീകരിക്കണം. Technical terms English-ൽ ഉപയോഗിക്കണം.

**Common mistake / precaution:** Do not add magnitudes directly when phase angles differ.

## 2. Pure R, L and C AC circuits–

In pure resistance, voltage/current are in phase. In inductance, current lags voltage; in capacitance, current leads voltage. Phasor diagrams and waveforms express these relationships.

### Study and application method

Draw one reference phasor, mark lead/lag by  $90^\circ$ , calculate reactance/impedance and identify power implication.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Draw one reference phasor, mark lead/lag by  $90^\circ$ , calculate reactance/impedance and identify power implication.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept എങ്ങനെ എങ്ങനെ എങ്ങനെ. എന്ത് diagram / circuit / formula / procedure എങ്ങനെ എങ്ങനെ. എങ്ങനെ result എങ്ങനെ application എങ്ങനെ എങ്ങനെ എങ്ങനെ. Technical terms English-  
എങ്ങനെ എങ്ങനെ.

**Common mistake / precaution:** Reactance is frequency dependent; do not treat it as fixed DC resistance.

## 3. RL, RC and RLC series circuits and power–

Series AC circuits combine resistance and reactance vectorially. Impedance triangle, power triangle and power factor relate voltage/current phase difference to active, reactive and apparent power.

### Study and application method

Compute R and net reactance, form impedance, find current and then calculate P, Q, S and power factor with units.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Compute R and net reactance, form impedance, find current and then calculate P, Q, S and power factor with units.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ പ്രശ്നം പരിഹരിക്കാൻ ഉപയോഗിക്കണം. ഈ diagram / circuit / formula / procedure ഈ പ്രശ്നം പരിഹരിക്കാൻ ഉപയോഗിക്കണം. ഈ result ഈ പ്രശ്നം പരിഹരിക്കാൻ ഉപയോഗിക്കണം. Technical terms English-  
ഈ പ്രശ്നം പരിഹരിക്കാൻ ഉപയോഗിക്കണം.

**Common mistake / precaution:** Power factor sign/convention must agree with lagging inductive or leading capacitive load.

**Module 2 revision cue:** Re-read official major topics, redraw one key diagram/flow and explain one practical or numerical method without looking at notes.

### MODULE 3

## Resonance and Parallel AC Circuits

Series resonance, Q factor and bandwidth; admittance/conductance/susceptance; two-branch parallel circuits; parallel resonance and applications.

7 L + 8 T hours

CO3

Understand · Apply

### Learning goals


Identify core terms, explain the principle and complete the stated application or practical outcome.

### Key evidence

Use a labelled diagram, table, graph, procedure or calculation that matches the topic.
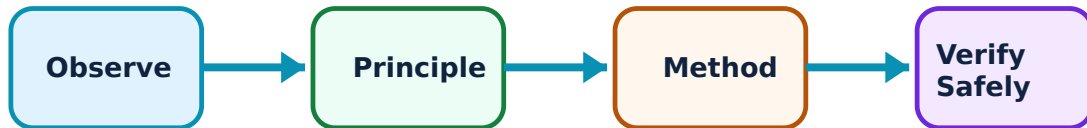
## Engineering habit

Check units, polarity/direction, ratings, materials and safety before concluding.



Study flow for Resonance and Parallel AC Circuits: identify the system, state its principle, follow the correct method and verify the result safely.

### 1. Series RLC resonance–

At series resonance inductive and capacitive reactances cancel, leaving minimum impedance in ideal series circuit. Resonant frequency, Q factor and bandwidth describe frequency response.

#### Study and application method

State resonance condition, calculate resonant frequency/Q from permitted formulas and relate bandwidth to resonant frequency and Q.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

#### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** State resonance condition, calculate resonant frequency/Q from permitted formulas and relate bandwidth to resonant frequency and Q.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഫലം concept ഫലം diagram / circuit / formula / procedure ഫലം result application ഫലം Technical terms English-ഫലം ഫലം.

**Common mistake / precaution:** Resonance does not mean every voltage in a circuit is small; reactive element voltages can be significant.

## 2. Admittance and parallel-circuit solution–

Admittance is reciprocal of impedance; conductance and susceptance are its real and imaginary components. Parallel circuits are efficiently solved by adding branch admittances or using vector methods.

### Study and application method

Convert each branch to admittance, add components, find total current/phase and verify branch-current sum.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.



## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Convert each branch to admittance, add components, find total current/phase and verify branch-current sum.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതെങ്കിലും concept നോക്കുക. ഏതെങ്കിലും diagram / circuit / formula / procedure നോക്കുക. ഏതെങ്കിലും result നോക്കുക. application നോക്കുക. Technical terms English-  
നോക്കുക.

**Common mistake / precaution:** Keep conductance and susceptance signs consistent; capacitive and inductive susceptances oppose.

## 3. Parallel resonance and comparison–

Parallel resonance has a different impedance/current behaviour from series resonance. The syllabus compares them and asks applications of resonant circuits.

### Study and application method

Use a comparison table for impedance, supply current, current/voltage magnification, frequency response and common use.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Use a comparison table for impedance, supply current, current/voltage magnification, frequency response and common use.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ ചോദ്യം പരിഹരിക്കാൻ ഉപയോഗിക്കണം. ഈ diagram / circuit / formula / procedure ഉപയോഗിക്കണം. ഏതു result ഉണ്ടാകും എന്നതിന്റെ application പരിശോധിക്കുക. Technical terms English-ൽ എഴുതുക.

**Common mistake / precaution:** Do not assume a series-resonance graph applies to a parallel circuit.

**Module 3 revision cue:** Re-read official major topics, redraw one key diagram/flow and explain one practical or numerical method without looking at notes.

## MODULE 4

# Three-Phase AC Systems

Three-phase generation/waveforms/phasors/sequence; star/delta connections; balanced-system calculations and power.

9.5 L + 5.5 T hours

CO4

Understand · Apply

## Learning goals

Identify core terms, explain the principle and complete the stated application or practical outcome.

## Key evidence

Use a labelled diagram, table, graph, procedure or calculation that matches the topic.

## Engineering habit

Check units, polarity/direction, ratings, materials and safety before concluding.



Study flow for Three-Phase AC Systems: identify the system, state its principle, follow the correct method and verify the result safely.

## 1. Three-phase generation and phase sequence–

A three-phase generator produces three equal-frequency voltages displaced by  $120^\circ$ . Waveforms and phasors show sequence and balanced-system relationship. Three-phase systems offer practical advantages in power transmission and machines.

### Study and application method

Draw three phase waveforms/phasors with sequence marked, then state one operational advantage over single phase.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Draw three phase waveforms/phasors with sequence marked, then state one operational advantage over single phase.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ ചോദ്യത്തിന് ഉപയോഗിക്കണം. ഈ diagram / circuit / formula / procedure ഉപയോഗിക്കണം. ഈ result ഉപയോഗിക്കണം application ഉപയോഗിക്കണം. Technical terms English-ൽ ഉപയോഗിക്കണം.

**Common mistake / precaution:** Changing phase sequence can reverse motor rotation; sequence is not only a drawing convention.

## 2. Star and delta interconnections–

Star and delta connect three phase elements differently. In balanced systems, line/phase voltage and current relations are derived using vector diagrams, and networks are solved from these relations.

### Study and application method

State connection, identify line/phase quantities, draw vector relation and use correct  $\sqrt{3}$  factor with a labelled derivation.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** State connection, identify line/phase quantities, draw vector relation and use correct  $\sqrt{3}$  factor with a labelled derivation.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept എങ്ങനെ എങ്ങനെ എങ്ങനെ. എന്ത് diagram / circuit / formula / procedure എങ്ങനെ എങ്ങനെ. എങ്ങനെ result എങ്ങനെ application എങ്ങനെ എങ്ങനെ എങ്ങനെ. Technical terms English-  
എങ്ങനെ എങ്ങനെ.

**Common mistake / precaution:** Do not interchange star voltage relation with delta current relation.

## 3. Three-phase power—

Balanced three-phase systems have active, reactive and apparent power related to line quantities and power factor. The same physical definitions apply but with three-phase relation.

### Study and application method

Identify balanced connection, calculate requested line/phase value, then use appropriate power expression and state unit/power factor.

Connect the explanation to the official student learning outcome before attempting a numerical, diagram, procedure or viva answer.

### Evidence of understanding

Use correct terminology, a labelled sketch/table where useful, correct units or conditions, and a conclusion linked to the observed or calculated result.

## How to construct a complete answer

**Given:** identify the quantities, device condition, waveform or circuit arrangement.

**Required:** state exactly what must be found or explained.

**Method:** Identify balanced connection, calculate requested line/phase value, then use appropriate power expression and state unit/power factor.

**Answer habit:** show a labelled step, the relevant unit/condition and a short interpretation.

**Malayalam support:** ഏതു concept ഈ problem ഈ diagram / circuit / formula / procedure ഈ result ഈ application ഈ Technical terms English-ഈ ഈ.

**Common mistake / precaution:** Use line values only with the matching formula; show whether data are line or phase quantities.

**Module 4 revision cue:** Re-read official major topics, redraw one key diagram/flow and explain one practical or numerical method without looking at notes.

### FORMULA AND PROCEDURE BANK

## Rapid Recall Bank

### Recall 1

State symbols and SI units before substitution.

### Recall 2

Draw the circuit, system boundary, vector or process flow before reasoning.

### Recall 3

For laboratory work: aim → apparatus → diagram → procedure → observation → calculation → result → precautions.

### Recall 4

For a graph: label axes, units, scale, operating region and conclusion.

### Recall 5

For a comparison: use construction, working, result, advantage and limitation.

### Recall 6

For an extended answer: definition/principle, labelled diagram, working steps, application and a caution/limitation.

#### DIAGRAM LIBRARY

### Diagram Library for Rapid Revision

#### Module 1: Electric Circuits and Network Theorems

Use the concept flow to revise observation, principle, method and verification.

#### Module 2: Phasor Algebra and AC Series Circuits

Use the concept flow to revise observation, principle, method and verification.

#### Module 3: Resonance and Parallel AC Circuits

Use the concept flow to revise observation, principle, method and verification.

## Module 4: Three-Phase AC Systems

Use the concept flow to revise observation, principle, method and verification.

### SELF-LEARNING

## Official Self-Learning and Student Activities

### Structured activity

Solve KCL/KVL, mesh/nodal, network-theorem and star-delta problems.

Keep evidence in your record: date, source/observation, diagram/table, key learning and questions for discussion.

### Structured activity

Practise polar/rectangular phasor operations and AC power-factor calculations.

Keep evidence in your record: date, source/observation, diagram/table, key learning and questions for discussion.

### Structured activity

Compare series/parallel resonance and solve two-branch circuits by admittance/vector methods.

Keep evidence in your record: date, source/observation, diagram/table, key learning and questions for discussion.

### Structured activity

Draw three-phase phasors and calculate balanced star/delta system parameters and power.

Keep evidence in your record: date, source/observation, diagram/table, key learning and questions for discussion.

**Activity discipline:** The supplied PDF assigns the listed self-learning hours. This handbook preserves the activity direction; the teacher's approved schedule and safety



## EXAMINATION READINESS

# Assessment Methodology and Examination Pattern

| Official assessment structure |                            |                                                       |
|-------------------------------|----------------------------|-------------------------------------------------------|
| Component                     | Official mark / conversion | Student evidence                                      |
| Attendance                    | 5 marks                    | End-of-semester attendance component.                 |
| Self-learning activities      | 15 marks                   | Module-linked activities.                             |
| Series examinations           | 20 + 20 converted          | Two 50-mark series examinations.                      |
| CIE total                     | Theory CIE 40              | Continuous internal evaluation.                       |
| Written ESE                   | Theory ESE 60              | 2.5 hours; official Part A / Part B / Part C pattern. |

## Series-test pattern

The supplied theory pattern uses Part A (1-mark), Part B (3-mark with choice) and Part C (7-mark) distribution across the stated modules. Practical courses follow the supplied practical-test scheme.

## Examination evidence

Show a complete method, correct units/conditions, clear diagrams or tables, a result/conclusion and safety awareness for any apparatus or process involved.

## EXAM PRACTICE

# Module-wise Questions with Answers

## Module 1 — Electric Circuits and Network Theorems

**Explain Circuit fundamentals and Kirchhoff laws and state one correct method, application or precaution. –**

Circuit analysis uses branch, node, loop, current, voltage, source and reference direction consistently. Kirchhoff's current law expresses charge conservation at a node; Kirchhoff's voltage law expresses algebraic voltage balance around a loop.

**Answer framework:** Assign current/voltage directions, write equations with a consistent sign convention, solve maximum-three-loop systems and interpret negative result as reversed assumed direction.

**Important point:** Do not mix reference directions midway through an equation set.

**Explain Mesh and nodal analysis and state one correct method, application or precaution. –**

Mesh analysis uses loop currents; nodal analysis uses node voltages. Both transform a circuit into simultaneous equations and are limited to the stated complexity in the syllabus.

**Answer framework:** Choose method that gives fewer unknowns, label circuit clearly, write independent equations and verify one result using KCL/KVL.

**Important point:** A current source or voltage source may require special treatment; identify it before writing equations.

**Explain Network theorems and star-delta conversion and state one correct method, application or precaution. –**

Superposition, Thevenin, Norton and maximum-power-transfer theorems simplify linear network analysis. Star-delta conversion replaces a three-terminal network with an equivalent form for simple DC circuits.

**Answer framework:** State theorem, deactivate only independent sources where appropriate, determine equivalent seen at load terminals and then restore load/result.

**Important point:** Superposition applies to voltage/current, not directly to power; calculate power after final response.

## Module 2 — Phasor Algebra and AC Series Circuits

**Explain Phasors and complex-number representation and state one correct method, application or precaution. –**

A phasor represents sinusoidal magnitude and phase at common frequency. The  $j$  operator represents a ninety-degree rotation. Rectangular and polar forms support different calculations.

**Answer framework:** Convert consistently between forms, add/subtract in rectangular form and multiply/divide in polar form, then state final magnitude/angle.

**Important point:** Do not add magnitudes directly when phase angles differ.

**Explain Pure R, L and C AC circuits and state one correct method, application or precaution.–**

In pure resistance, voltage/current are in phase. In inductance, current lags voltage; in capacitance, current leads voltage. Phasor diagrams and waveforms express these relationships.

**Answer framework:** Draw one reference phasor, mark lead/lag by  $90^\circ$ , calculate reactance/impedance and identify power implication.

**Important point:** Reactance is frequency dependent; do not treat it as fixed DC resistance.

**Explain RL, RC and RLC series circuits and power and state one correct method, application or precaution.–**

Series AC circuits combine resistance and reactance vectorially. Impedance triangle, power triangle and power factor relate voltage/current phase difference to active, reactive and apparent power.

**Answer framework:** Compute R and net reactance, form impedance, find current and then calculate P, Q, S and power factor with units.

**Important point:** Power factor sign/convention must agree with lagging inductive or leading capacitive load.

## Module 3 — Resonance and Parallel AC Circuits

**Explain Series RLC resonance and state one correct method, application or precaution.–**

At series resonance inductive and capacitive reactances cancel, leaving minimum impedance in ideal series circuit. Resonant frequency, Q factor and bandwidth describe frequency response.

**Answer framework:** State resonance condition, calculate resonant frequency/Q from permitted formulas and relate bandwidth to resonant frequency and Q.

**Important point:** Resonance does not mean every voltage in a circuit is small; reactive element voltages can be significant.

**Explain Admittance and parallel-circuit solution and state one correct method, application or precaution.–**

Admittance is reciprocal of impedance; conductance and susceptance are its real and imaginary components. Parallel circuits are efficiently solved by adding branch admittances or using vector methods.

**Answer framework:** Convert each branch to admittance, add components, find total current/phase and verify branch-current sum.

**Important point:** Keep conductance and susceptance signs consistent; capacitive and inductive susceptances oppose.

**Explain Parallel resonance and comparison and state one correct method, application or precaution.–**

Parallel resonance has a different impedance/current behaviour from series resonance. The syllabus compares them and asks applications of resonant circuits.

**Answer framework:** Use a comparison table for impedance, supply current, current/voltage magnification, frequency response and common use.

**Important point:** Do not assume a series-resonance graph applies to a parallel circuit.

## **Module 4 — Three-Phase AC Systems**

**Explain Three-phase generation and phase sequence and state one correct method, application or precaution.–**

A three-phase generator produces three equal-frequency voltages displaced by  $120^\circ$ . Waveforms and phasors show sequence and balanced-system relationship. Three-phase systems offer practical advantages in power transmission and machines.

**Answer framework:** Draw three phase waveforms/phasors with sequence marked, then state one operational advantage over single phase.

**Important point:** Changing phase sequence can reverse motor rotation; sequence is not only a drawing convention.

**Explain Star and delta interconnections and state one correct method, application or precaution.–**

Star and delta connect three phase elements differently. In balanced systems, line/phase voltage and current relations are derived using vector diagrams, and networks are solved from these relations.

**Answer framework:** State connection, identify line/phase quantities, draw vector relation and use correct  $\sqrt{3}$  factor with a labelled derivation.

**Important point:** Do not interchange star voltage relation with delta current relation.

### Explain Three-phase power and state one correct method, application or precaution. –

Balanced three-phase systems have active, reactive and apparent power related to line quantities and power factor. The same physical definitions apply but with three-phase relation.

**Answer framework:** Identify balanced connection, calculate requested line/phase value, then use appropriate power expression and state unit/power factor.

**Important point:** Use line values only with the matching formula; show whether data are line or phase quantities.

#### PRACTICE ONLY

### Practice Model Paper

**Important:** This practice paper is based on the official pattern in the supplied syllabus. It is **not** an official SITTR model question paper.

#### Part A — short response

1. State one key definition from Module 1: Electric Circuits and Network Theorems.
2. Identify one diagram, observation, formula or safety condition relevant to Module 1.
3. State one key definition from Module 2: Phasor Algebra and AC Series Circuits.
4. Identify one diagram, observation, formula or safety condition relevant to Module 2.
5. State one key definition from Module 3: Resonance and Parallel AC Circuits.
6. Identify one diagram, observation, formula or safety condition relevant to Module 3.
7. State one key definition from Module 4: Three-Phase AC Systems.
8. Identify one diagram, observation, formula or safety condition relevant to Module 4.

## Part B — structured explanation

1. Explain a selected procedure/principle from Module 1 with a labelled diagram, table or method.
2. Explain a selected procedure/principle from Module 2 with a labelled diagram, table or method.
3. Explain a selected procedure/principle from Module 3 with a labelled diagram, table or method.
4. Explain a selected procedure/principle from Module 4 with a labelled diagram, table or method.

## Part C — extended response / practical task

1. Develop a complete answer or practical plan for: Circuit types/terms, Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta conversion..
2. Develop a complete answer or practical plan for:  $j$  operator, phasor rectangular/polar conversion and operations; pure R/L/C, RL/RC/RLC, impedance, power and power factor..
3. Develop a complete answer or practical plan for: Series resonance, Q factor and bandwidth; admittance/conductance/susceptance; two-branch parallel circuits; parallel resonance and applications..
4. Develop a complete answer or practical plan for: Three-phase generation/waveforms/phasors/sequence; star/delta connections; balanced-system calculations and power..

### LAST-MILE REVISION

## Quick Revision

### Module 1: Electric Circuits and Network Theorems

Circuit types/terms, Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta conversion.

- Match each topic to CO1.
- Redraw or rehearse one key method.
- Check one common mistake/precaution.

### Module 2: Phasor Algebra and AC Series Circuits

$j$  operator, phasor rectangular/polar conversion and operations; pure R/L/C, RL/RC/RLC, impedance, power and power factor.

- Match each topic to CO2.
- Redraw or rehearse one key method.

- Check one common mistake/precaution.

### Module 3: Resonance and Parallel AC Circuits

Series resonance, Q factor and bandwidth; admittance/conductance/susceptance; two-branch parallel circuits; parallel resonance and applications.

- Match each topic to CO3.
- Redraw or rehearse one key method.
- Check one common mistake/precaution.

### Module 4: Three-Phase AC Systems

Three-phase generation/waveforms/phasors/sequence; star/delta connections; balanced-system calculations and power.

- Match each topic to CO4.
- Redraw or rehearse one key method.
- Check one common mistake/precaution.

**Common mistakes:** Writing an unlabelled diagram; ignoring units, polarity or conditions; treating a practical result as valid without observations; confusing a definition with an application; and omitting a safety precaution where the topic uses apparatus, current, heat, chemicals or tools.

**Exam checklist:** Read the command word; answer every part; draw clean labelled diagrams; use a clear calculation/procedure; state result with units or observation; and reserve two minutes for checking.

#### VOCABULARY

### Glossary

## Important terms from the syllabus

| Term / topic                               | One-line meaning                                                                                                   |
|--------------------------------------------|--------------------------------------------------------------------------------------------------------------------|
| Circuit fundamentals and Kirchhoff laws    | Circuit analysis uses branch, node, loop, current, voltage, source and reference direction consistently.           |
| Mesh and nodal analysis                    | Mesh analysis uses loop currents; nodal analysis uses node voltages.                                               |
| Network theorems and star-delta conversion | Superposition, Thevenin, Norton and maximum-power-transfer theorems simplify linear-network analysis.              |
| Phasors and complex-number representation  | A phasor represents sinusoidal magnitude and phase at common frequency.                                            |
| Pure R, L and C AC circuits                | In pure resistance, voltage/current are in phase.                                                                  |
| RL, RC and RLC series circuits and power   | Series AC circuits combine resistance and reactance vectorially.                                                   |
| Series RLC resonance                       | At series resonance inductive and capacitive reactances cancel, leaving minimum impedance in ideal series circuit. |
| Admittance and parallel-circuit solution   | Admittance is reciprocal of impedance; conductance and susceptance are its real and imaginary components.          |
| Parallel resonance and comparison          | Parallel resonance has a different impedance/current behaviour from series resonance.                              |
| Three-phase generation and phase sequence  | A three-phase generator produces three equal-frequency voltages displaced by $120^\circ$ .                         |
| Star and delta interconnections            | Star and delta connect three phase elements differently.                                                           |
| Three-phase power                          | Balanced three-phase systems have active, reactive and apparent power related to line quantities and power factor. |

## LEARNING RESOURCES

### References

#### Officially listed print resources

1. B. L. Theraja and A. K. Theraja, A Text Book of Electrical Technology Vol. I.
2. V. K. Mehta and Rohit Mehta, Principles of Electrical Engineering.
3. B. R. Gupta and Vandana Singhal, Fundamentals of Electrical Network.

#### Officially listed web resources

- <https://www.swayam.gov.in>
- <https://www.electrical4u.com>
- <https://www.vlab.co.in>



Links are reproduced because they appear in the supplied syllabus. Use institutional safety and access guidance when opening external resources.