



# Electric Circuits and Systems

This course develops systematic DC and AC circuit analysis using Kirchhoff laws, mesh/nodal methods, network theorems, phasor algebra, resonance and balanced three-phase systems. Numerical problem-solving and phasor interpretation are central.

REV2026

Semester II

Theory + Tutorial

Malayalam support

Printable handbook

|               |                   |
|---------------|-------------------|
| Course code   | 2032              |
| Semester      | II                |
| Course type   | Theory + Tutorial |
| Contact hours | 60                |
| Credits       | 4                 |
| CIE / ESE     | 40 / 60           |
| Modules       | 4                 |

## COURSE OVERVIEW

### What this handbook covers

The structure follows the supplied official SITTTTR Kerala Revision 2026 syllabus. It is a learning handbook rather than a replacement for the official syllabus PDF. Use the module checklist to ensure that every prescribed point has been revised.

#### CO1

Solve DC networks using Kirchhoff laws, mesh/nodal analysis, network theorems and star-delta transformation.

#### CO2

### CO3

Analyse series/parallel resonance and two-branch parallel AC circuits.

### CO4

Analyse balanced star/delta three-phase systems and compute line/phase quantities and power.

## Module roadmap

**Module I**  
**Electric circuits and network theorems**


**Module II**  
**Phasor algebra and series AC circuits**

**Module III**  
**Resonance and parallel AC circuits**

**Module IV**  
**Balanced three-phase AC systems**

## VISUAL CONCEPT

## See the subject as a system

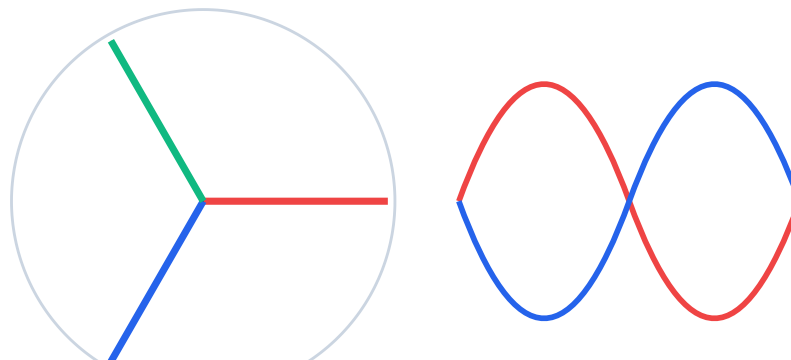

Balanced phasors are displaced by  $120^\circ$

## MODULE I

15 (3.5 L + 11.5 T)

CO1

## Electric circuits and network theorems

KCL node-ൽ current conservation ആണ്; KVL closed loop-ൽ voltage conservation ആണ്. Sign convention ഒരിക്കൽ തിരഞ്ഞെടുക്കുക, equation മുഴുവൻ അതേ രീതിയിൽ പാലിക്കുക. Thevenin/Norton equivalent load മാറ്റുമ്പോൾ analysis വേഗത്തിലാക്കുന്നു.

## Circuit types and terms

Identify active/passive, linear/nonlinear, bilateral/unilateral, lumped/distributed and independent/dependent-source circuits. Define branch, node, loop and mesh.

## Kirchhoff current and voltage laws

Write algebraic current sum at a node and voltage sum around a loop. Establish current directions and voltage polarities before equations.

## Mesh analysis

Assign mesh currents, write self and mutual resistance terms and solve up to three simultaneous equations using elimination, matrices or Cramer's rule.

## Nodal analysis

Choose a reference node, express branch currents in node voltages and solve up to three unknown node voltages.

## Superposition theorem

In a linear network, consider one independent source at a time: ideal voltage sources become shorts and ideal current sources become opens. Power is not superposed directly.

## Thevenin theorem

Remove the load, calculate open-circuit  $V_{th}$  and equivalent resistance  $R_{th}$  with independent sources deactivated, then reconnect the load.

## Norton theorem

Find short-circuit current  $I_N$  and equivalent  $R_N = R_{th}$ . Convert between Thevenin and Norton forms using  $V_{th} = I_N R_{th}$ .

## Maximum power transfer

For DC resistive networks, maximum load power occurs at  $R_L = R_{th}$ ; efficiency is 50% at that condition.

## Star-delta transformation

Convert three-terminal resistor networks without derivation and use the conversion to reduce otherwise non-series/parallel DC circuits.

## Rules / common mistakes

- Mark assumed directions; a negative answer means opposite direction.
- Deactivate only independent sources when finding equivalent resistance.
- Never short an ideal voltage source in the original live circuit.
- Check power balance where practical.

- Solve one three-mesh and one three-node network.
- Verify superposition against direct Kirchhoff solution.
- Solve the same load using Thevenin and Norton equivalents.
- Reduce a bridge section using star-delta conversion.

Course 2032

## MODULE II

15 (10 L + 5 T)

CO2

# Phasor algebra and series AC circuits

Phasor sinusoidal steady-state quantity-യുടെ magnitude/phase representation ആണ്. R-ൽ voltage/current same phase; L-ൽ current  $90^\circ$  lag; C-ൽ current  $90^\circ$  lead. Complex-number sign തെറ്റിയാൽ power factor തെറ്റും.

### j operator and complex plane

$j = \sqrt{-1}$  represents  $90^\circ$  rotation. Use rectangular  $a + jb$  for addition/subtraction and polar  $M\angle\theta$  for multiplication/division.

### Rectangular-polar conversion

$M = \sqrt{a^2 + b^2}$ ,  $\theta = \text{atan2}(b, a)$ ;  $a = M \cos\theta$  and  $b = M \sin\theta$ . Preserve the correct quadrant.

### Pure resistance

$Z = R$ , current and voltage are in phase,  $P = VI$  and  $Q = 0$ .

### Pure inductance

$XL = \omega L$ ,  $Z = jXL$ , current lags voltage by  $90^\circ$  and average active power is zero ideally.

### Pure capacitance

$XC = 1/(\omega C)$ ,  $Z = -jXC$ , current leads voltage by  $90^\circ$  and average active power is zero ideally.

### Series RL, RC and RLC

Add impedances as complex numbers. Draw phasor diagram and impedance triangle; calculate current, phase angle and power factor.

### Power triangle

Active  $P = VI \cos\phi$ , reactive  $Q = VI \sin\phi$  and apparent  $S = VI$ ;  $S^2 = P^2 + Q^2$ . Identify leading or lagging power factor.

### Series-circuit problems

Compute element voltages, total impedance, current and power. Verify that phasor voltages add to the supply.

## Rules / common mistakes

- Use RMS values for AC power unless stated otherwise.
- Keep inductive reactance positive  $j$  and capacitive reactance negative  $j$ .
- Use  $\text{atan2}$  or quadrant correction.

- State whether power factor is leading or lagging

Course 2032

## Practice and self-learning

- Convert five phasors between polar and rectangular form.
- Solve pure R/L/C and series RL/RC/RLC circuits.
- Draw impedance and power triangles from numerical results.

MODULE III

15 (7 L + 8 T)

C03

# Resonance and parallel AC circuits

Series resonance-ൽ  $X_L = X_C$ , impedance minimum, current maximum. Parallel resonance-ൽ input current minimum/impedance maximum എന്നതാണ് സാധാരണ behaviour. Q factor selectivity കാണിക്കുന്നു; bandwidth =  $f_r/Q$ .

## Series resonance

For a series RLC circuit, resonance occurs when  $X_L = X_C$  and net reactance is zero. Derive  $f_r = 1/(2\pi\sqrt{LC})$ .

## Q factor

For series resonance  $Q = \omega_r L/R = 1/(\omega_r CR)$ . Explain voltage magnification and selectivity.

## Bandwidth

$BW = f_2 - f_1 = f_r/Q$  for the standard series response. Define half-power frequencies.

## Admittance quantities

$Y = 1/Z$  in siemens, G is conductance and B is susceptance. Inductive susceptance is negative and capacitive susceptance positive under the usual convention.

## Two-branch parallel circuits

Solve by admittance: add branch conductance and susceptance, find total Y, invert for Z and calculate source current. Also solve by rectangular/vector current addition.

## Parallel resonance

State the applicable resonant-frequency expression for the circuit form given and explain circulating branch currents, high impedance and low supply current.

## Series versus parallel resonance

Compare input impedance, source current, magnification, typical response and applications.

## Applications

Tuning, filters, oscillators, impedance selection and frequency-sensitive networks.

## Rules / common mistakes

- Do not use the series-resonance formula blindly for every parallel circuit topology.
- Add admittances in parallel, not impedances.
- Keep susceptance signs consistent.
- Q and bandwidth relations depend on the stated circuit model.

## Practice and self-learning

- Calculate  $f_r$ , Q and BW for a series RLC circuit.
- Solve two parallel branches by admittance and vector-current methods and compare.
- Sketch current/impedance frequency responses.

## MODULE IV

15 (9.5 L + 5.5 T)

CO4

# Balanced three-phase AC systems

Three-phase voltages  $120^\circ$  apart ആണ്. Star connection-ൽ  $V_L = \sqrt{3} V_{ph}$ ,  $I_L = I_{ph}$ . Delta connection-ൽ  $V_L = V_{ph}$ ,  $I_L = \sqrt{3} I_{ph}$ . Line/phase relation mix ചെയ്യുന്നത് ഏറ്റവും സാധാരണ mistake ആണ്.

## Generation of three-phase voltage

Three identical windings displaced by  $120^\circ$  electrical degrees produce balanced phase voltages. Explain waveforms and phasor diagram.

## Phase sequence

ABC and ACB sequences determine rotating-field direction. Interchanging any two lines reverses sequence.

## Advantages of three phase

More constant power, economical conductor use, self-starting motors and compact machines for a given output.

## Star connection

Common neutral point:  $V_L = \sqrt{3} V_{ph}$  with  $30^\circ$  displacement;  $I_L = I_{ph}$  for a balanced load.

## Delta connection

Closed loop:  $V_L = V_{ph}$  and  $I_L = \sqrt{3} I_{ph}$  with  $30^\circ$  displacement.

## Balanced-load problems

Calculate phase impedance, phase current, line current, line voltage and neutral current for balanced star/delta systems.

## Three-phase power

## Star-delta comparison

For balanced systems  $P = \sqrt{3} V_L I_L \cos\phi$ ,  $Q = \sqrt{3} V_L I_L \sin\phi$  and  $S = \sqrt{3} V_L I_L$ . These expressions apply to both star and delta when line quantities are used.

Compare insulation requirement, neutral availability, phase voltage/current and common applications.

## Rules / common mistakes

- Write connection type before selecting formulas.
- Use line quantities consistently in three-phase power formulas.
- Balanced-load neutral current is zero in star.
- Phase sequence is not the same as phase angle magnitude.

## Practice and self-learning

- Draw positive and negative phase-sequence phasors/waveforms.
- Solve balanced star and delta load problems.
- Calculate active, reactive and apparent three-phase power.

## QUICK REVISION

# Formula / rule bank

### Rule / Formula 1

KCL:  $\sum I = 0$  at a node

### Rule / Formula 2

KVL:  $\sum V = 0$  around a loop

### Rule / Formula 3

$V_{th}$  = open-circuit voltage;  $R_{th}$  = resistance seen at load terminals

### Rule / Formula 4

$I_N$  = short-circuit current;  $R_N = R_{th}$

### Rule / Formula 5

Maximum DC power:  $R_L = R_{th}$

### Rule / Formula 6

Star → Delta:  $R_{ab} = R_a + R_b + (R_a R_b / R_c)$ , cyclic

### Rule / Formula 7

Delta → Star:  $R_a = R_{ab} R_{ca} / (R_{ab} + R_{bc} + R_{ca})$

### Rule / Formula 8

$Z_R = R$ ;  $Z_L = j\omega L$ ;  $Z_C = 1/(j\omega C) = -j/(\omega C)$

### Rule / Formula 9

$Y = 1/Z = G + jB$

### Rule / Formula 10

$P = VI \cos \phi$ ;  $Q = VI \sin \phi$ ;  $S = VI$

### Rule / Formula 11

$f_r = 1/(2\pi\sqrt{LC})$

### Rule / Formula 12

Series  $Q = \omega rL/R = 1/(\omega rCR)$

### Rule / Formula 13

$BW = f_r/Q$

### Rule / Formula 14

Star:  $V_L = \sqrt{3}V_{ph}$ ,  $I_L = I_{ph}$

### Rule / Formula 15

Delta:  $V_L = V_{ph}$ ,  $I_L = \sqrt{3}I_{ph}$



## Rule / Formula 16

Three-phase  $P = \sqrt{3}VLIL\cos\phi$ ;  $Q = \sqrt{3}VLIL\sin\phi$ ;  $S = \sqrt{3}VLIL$

## Worked checkpoints

### Worked checkpoint 1

A Thevenin source 12 V with  $R_{th} = 6 \Omega$  delivers maximum power to  $R_L = 6 \Omega$ ;  $P_{max} = V_{th}^2/(4R_{th}) = 6 \text{ W}$ .

### Worked checkpoint 2

For  $R = 8 \Omega$  and  $X_L = 6 \Omega$  in series,  $Z = 8 + j6 = 10 \angle 36.87^\circ \Omega$  and power factor = 0.8 lagging.

### Worked checkpoint 3

$L = 10 \text{ mH}$  and  $C = 100 \mu\text{F}$  gives  $f_r \approx 159.2 \text{ Hz}$ .

### Worked checkpoint 4

A balanced star load on 400 V line supply has  $V_{ph} = 400/\sqrt{3} \approx 231 \text{ V}$ .

## APPLICATION

# Practical, drawing and self-learning work

| No | Task                                                | Required evidence                                               |
|----|-----------------------------------------------------|-----------------------------------------------------------------|
| 1  | Three-mesh and nodal-analysis problem set.          | Record procedure, observation/result and safety/quality checks. |
| 2  | Superposition verification.                         | Record procedure, observation/result and safety/quality checks. |
| 3  | Thevenin/Norton load analysis.                      | Record procedure, observation/result and safety/quality checks. |
| 4  | Maximum-power and star-delta problems.              | Record procedure, observation/result and safety/quality checks. |
| 5  | Phasor conversion and operations.                   | Record procedure, observation/result and safety/quality checks. |
| 6  | Pure R/L/C and series AC problems.                  | Record procedure, observation/result and safety/quality checks. |
| 7  | Impedance and power triangles.                      | Record procedure, observation/result and safety/quality checks. |
| 8  | Series resonance calculations and response sketch.  | Record procedure, observation/result and safety/quality checks. |
| 9  | Parallel two-branch circuits by two methods.        | Record procedure, observation/result and safety/quality checks. |
| 10 | Parallel-resonance comparison.                      | Record procedure, observation/result and safety/quality checks. |
| 11 | Three-phase generation/sequence diagrams.           | Record procedure, observation/result and safety/quality checks. |
| 12 | Balanced star/delta and three-phase power problems. | Record procedure, observation/result and safety/quality checks. |

### EXAM PREPARATION

## Expected questions and model-answer guides

These are syllabus-aligned practice questions, not a claim about the exact end-semester paper.

2 marks

**Q1. Define branch, node, loop and mesh.**

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

2 marks

**Q2. State and apply KCL and KVL.**

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

2 marks

**Q3. Explain mesh and nodal analysis for up to three unknowns.**

## Model-answer guide

Course 2032

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

2 marks

### Q4. State limitations and procedure of superposition theorem.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

5 marks

### Q5. Derive/use Thevenin and Norton equivalents.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

5 marks

### Q6. State maximum power transfer theorem and solve a problem.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

5 marks

### Q7. Convert star to delta and delta to star.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

5 marks

### Q8. Explain $j$ operator and phasor conversion.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

5 marks

### Q9. Analyse pure R, L and C under AC.

## Model-answer guide

Course 2032

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q10. Solve a series RLC circuit and draw impedance/power triangles.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q11. Derive resonant frequency of series RLC.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q12. Define Q factor and bandwidth.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q13. Solve a two-branch parallel AC circuit using admittance.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q14. Compare series and parallel resonance.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q15. Explain generation and phase sequence of three-phase voltage.

## Model-answer guide

Course 2032

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q16. Derive line/phase relations in star and delta.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

8-10 marks

### Q17. Calculate balanced three-phase active, reactive and apparent power.

#### Model-answer guide

Answer using the definition/principle, a labelled diagram or formula where applicable, the ordered procedure/derivation, and one verification or application point. Cover the official module wording exactly.

## COVERAGE AUDIT

# Official syllabus coverage checklist

- Module I: Circuit types and terms
- Module I: Kirchhoff current and voltage laws
- Module I: Mesh analysis
- Module I: Nodal analysis
- Module I: Superposition theorem
- Module I: Thevenin theorem
- Module I: Norton theorem
- Module I: Maximum power transfer
- Module I: Star-delta transformation
- Module II: j operator and complex plane
- Module II: Rectangular-polar conversion
- Module II: Pure resistance
- Module II: Pure inductance
- Module II: Pure capacitance
- Module II: Series RL, RC and RLC
- Module II: Power triangle
- Module II: Series-circuit problems
- Module III: Series resonance
- Module III: Q factor
- Module III: Bandwidth

- Module III: Admittance quantities

Course 2032

- Module III: Two-branch parallel circuits
- Module III: Parallel resonance
- Module III: Series versus parallel resonance
- Module III: Applications
- Module IV: Generation of three-phase voltage
- Module IV: Phase sequence
- Module IV: Advantages of three phase
- Module IV: Star connection
- Module IV: Delta connection
- Module IV: Balanced-load problems
- Module IV: Three-phase power
- Module IV: Star-delta comparison

## REFERENCES

# Learning resources

1. A Textbook of Electrical Technology Vol. I — B. L. Theraja & A. K. Theraja
2. Principles of Electrical Engineering — V. K. Mehta & Rohit Mehta
3. Basic Electrical Engineering — V. Mittal & Arvind Mittal
4. Fundamentals of Electrical Network — B. R. Gupta & Vandana Singhal
5. Circuit Theory: Analysis and Synthesis — Abhijit Chakrabarti

Primary authority for scope: supplied official SITTTR Kerala Diploma Curriculum Revision 2026 syllabus PDF for Course 2032.